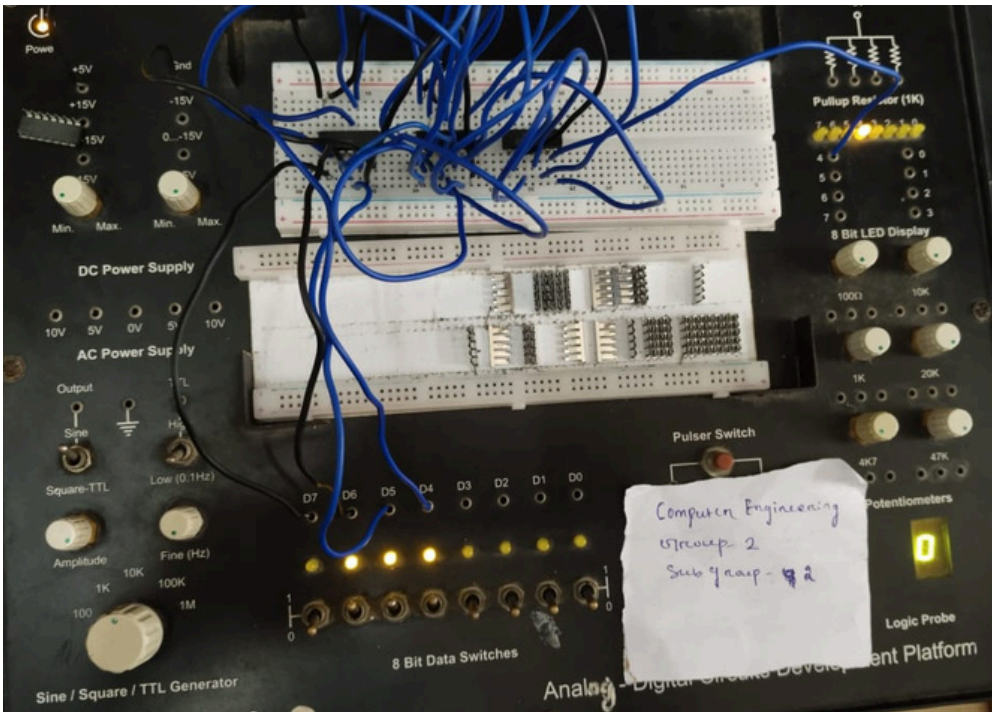
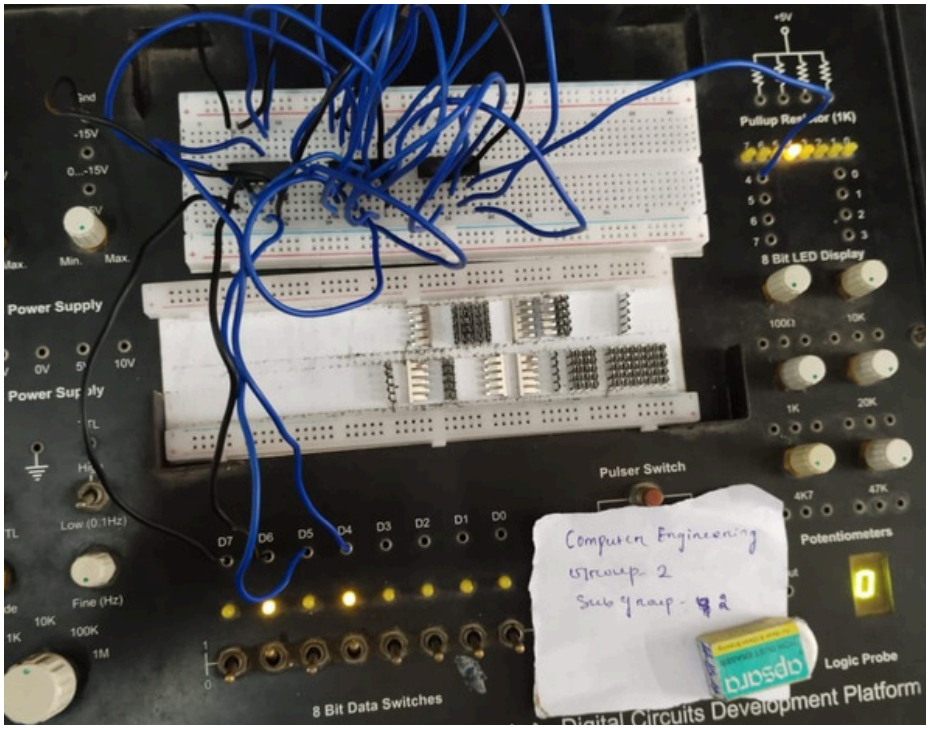
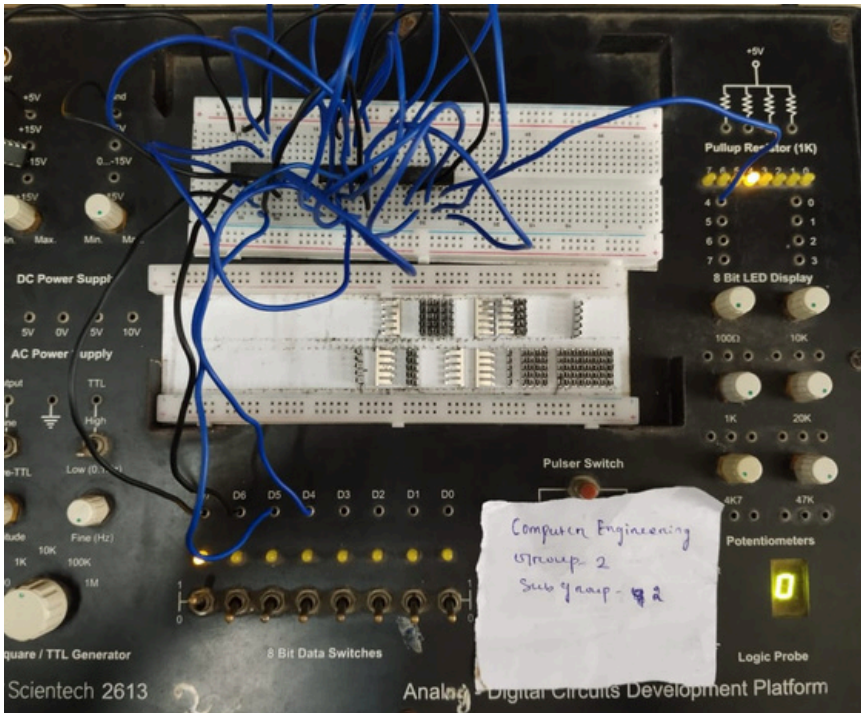
A<B


DC Power Supply
AC Power Supply
Sine / Square / TTL Generator
8 Bit Data Switches
Pulser Switch
8 Bit LED Display
Potentiometers
Logic Probe
Computer Engineering
Group- 2

A=B


Power Supply
8 Bit Data Switches
Pulser Switch
8 Bit LED Display
Potentiometers
Logic Probe
Computer Engineering
Group- 2
Digital Circuits Development Platform

A>B


DC Power Supply
AC Power Supply
8 Bit Data Switches
Pulser Switch
8 Bit LED Display
Potentiometers
Logic Probe
Computer Engineering
Group- 2
Scientech 2613
Digital Circuits Development Platform